

Solutions to PS 7 Physics 201

1. The impedance of the circuit is given by

$$Z(\omega) = R + \frac{1}{i\omega C} + i\omega L \quad (1)$$

$$= R + i(\omega L - \frac{1}{\omega C}). \quad (2)$$

Noting the relation between the amplitudes, $|I| = |V|/|Z|$, we have

$$\frac{|I(\omega)|}{|I_{\max}|} = \frac{|I(\omega)|}{|I(\omega_0)|} = \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}. \quad (3)$$

When $\omega = \omega_0 \pm \delta = \omega_0 \pm R/2L$, provided $\delta/\omega_0 \ll 1$, we have

$$\frac{|I(\omega_0 \pm \delta)|}{|I_{\max}|} = \frac{R}{\sqrt{R^2 + \{(\omega_0 \pm \delta)L - \frac{1}{(\omega_0 \pm \delta)C}\}^2}} \quad (4)$$

$$= \frac{R}{\sqrt{R^2 + \{(\omega_0 \pm \delta)L - \frac{1}{\omega_0 C}(1 \mp \frac{\delta}{\omega_0})\}^2}} \quad (5)$$

$$= \frac{R}{\sqrt{R^2 + (\pm\delta L \pm \frac{1}{\omega_0 C} \frac{\delta}{\omega_0})^2}} \quad (6)$$

$$= \frac{R}{\sqrt{R^2 + (\frac{R}{2} \pm \frac{R}{2})^2}} \quad (7)$$

$$= \frac{1}{\sqrt{2}}. \quad (8)$$

2. From the relation $1/Z_{//} = \sum 1/Z_i$, we get

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{\frac{1}{i\omega C}} + \frac{1}{i\omega L} \quad (9)$$

$$= \frac{1}{R} + i\omega C - \frac{i}{\omega L}, \quad (10)$$

and therefore,

$$Z = \frac{1}{\frac{1}{R} + i\omega C - \frac{i}{\omega L}} = \frac{R\omega L}{\omega L + i(\omega^2 CL - 1)R}. \quad (11)$$

3. The impedance of the circuit element shown in the figure satisfies the relation

$$\frac{1}{Z} = \frac{1}{\frac{1}{i\omega C}} + \frac{1}{R + i\omega L} \quad (12)$$

$$= i\omega C + \frac{1}{R + i\omega L} \quad (13)$$

$$= i\omega C + \frac{R - i\omega L}{R^2 + \omega^2 L^2} \quad (14)$$

$$= \frac{R + i\{(R^2 + \omega^2 L^2)\omega C - \omega L\}}{R^2 + \omega^2 L^2}. \quad (15)$$

$$(16)$$

Noting that $\text{Im}[Z] = 0$ (Z is real.) $\Leftrightarrow \text{Im}[1/Z] = 0$, we have

$$\text{Im}[Z] = 0 \Leftrightarrow (R^2 + \omega^2 L^2)\omega C - \omega L = 0 \quad (17)$$

$$\Leftrightarrow (R^2 + \omega^2 L^2)C - L = 0, \text{ or } \omega = 0 \quad (18)$$

$$\Leftrightarrow \omega = 0, \sqrt{\frac{L - CR^2}{CL^2}}. \quad (19)$$

Of course, $\sqrt{\frac{L - CR^2}{CL^2}}$ is real only if $L > CR^2$. Otherwise, the impedance is real only for $\omega = 0$ (Note that $Z = \infty$ for $\omega = 0$).

4. As seen in problem 1, the impedance is given by

$$Z(\omega) = R + \frac{1}{i\omega C} + i\omega L \quad (20)$$

$$= R + i(\omega L - \frac{1}{\omega C}). \quad (21)$$

Clearly, $R_1 = 100 \, \Omega$ gives the minimum impedance, and $R_2 = 200 \, \Omega$ gives the maximum impedance. Next, we have to consider the imaginary part of the impedance. For $\omega = 2000$, we get

$$\omega L_1 - \frac{1}{\omega C_1} = 2000 \, \text{s}^{-1} \times 1 \, \text{mH} - \frac{1}{2000 \, \text{s}^{-1} \times 1 \, \mu\text{F}} = -498 \, \Omega, \quad (22)$$

$$\omega L_1 - \frac{1}{\omega C_2} = 2000 \, \text{s}^{-1} \times 1 \, \text{mH} - \frac{1}{2000 \, \text{s}^{-1} \times 100 \, \mu\text{F}} = -3 \, \Omega, \quad (23)$$

$$\omega L_2 - \frac{1}{\omega C_1} = 2000 \, \text{s}^{-1} \times 2 \, \text{mH} - \frac{1}{2000 \, \text{s}^{-1} \times 1 \, \mu\text{F}} = -496 \, \Omega, \quad (24)$$

and

$$\omega L_2 - \frac{1}{\omega C_2} = 2000 \text{ s}^{-1} \times 2 \text{ mH} - \frac{1}{2000 \text{ s}^{-1} \times 100 \text{ } \mu\text{F}} = -1 \text{ } \Omega. \quad (25)$$

Therefore, (R_1, C_2, L_2) gives the minimum impedance $|Z_{\min}| = \sqrt{100^2 + 1^2} \approx 100 \text{ } \Omega$, and (R_2, C_1, L_1) gives the maximum impedance $|Z_{\max}| = \sqrt{200^2 + 498^2} \approx 537 \text{ } \Omega$.

5. The impedance Z_2 at $\omega = 500$ is given by

$$Z_2(\omega = 500) = 15 \text{ } \Omega + \frac{1}{i \times 500 \text{ s}^{-1} \times 2 \text{ } \mu\text{F}} = (15 - 1000i) \text{ } \Omega \approx 1000.1 e^{-1.556i} \text{ } \Omega, \quad (26)$$

and the total impedance is

$$Z_{\text{tot}}(\omega = 500) = (25 - 1000i) \text{ } \Omega \approx 1000.3 e^{-1.545i} \text{ } \Omega. \quad (27)$$

Using these, we can calculate the power loss across Z_2 . However, we have to note that $P_2 = I_2 V_2 = \text{Re}[\tilde{I}_2] \text{Re}[\tilde{V}_2] \neq \text{Re}[\tilde{I}_2 \tilde{V}_2]$, where \tilde{A} is the imaginary expression of A . (Operations such as derivative or integration commute with an operation of taking $\text{Re}[\]$, that is, the order of operations does not matter. Actually, this fact makes use of complex number convenient for this kind of problems. However, multiplication does not commute with $\text{Re}[\]$. Also note that complex numbers are "imaginary" tool to make calculation easier and that physical quantities we can observe in experiments are always real.) Therefore,

$$P_2 \equiv I_2 V_2 = I(I Z_2) = \left(\frac{V}{Z_{\text{tot}}}\right) \frac{V Z_2}{Z_{\text{tot}}} \quad (28)$$

$$= \text{Re}\left[\frac{30e^{i500t}[\text{V}]}{1000.3 e^{-1.545i} \text{ } \Omega}\right] \text{Re}\left[\frac{30e^{i500t}[\text{V}](1000.1 e^{-1.556i} \text{ } \Omega)}{1000.3 e^{-1.545i} \text{ } \Omega}\right] \quad (29)$$

$$= 0.900 \text{Re}[e^{i(500t+1.545)}] \text{Re}[e^{i(500t-0.011)}] [\text{W}] \quad (30)$$

$$= 0.900 \cos(500t + 1.545) \cos(500t - 0.011) [\text{W}] \quad (31)$$

$$= 0.450 \{\cos(1000t + 1.534) + \cos 1.556\} [\text{W}] \quad (32)$$

$$(33)$$

Also from this, we can easily calculate

$$(\text{Time average of power loss}) = 0.450 \cos 1.556 = 6.66 \text{ mW}. \quad (34)$$

6. The electric field between the plates is

$$\mathbf{E}(r) = \begin{cases} \frac{V(t)}{d} & (r < a) \\ 0 & (r > a), \end{cases} \quad (35)$$

where $d = 2$ cm is the separation between the plates and $a = 4$ cm is a radius of the plates. Noting that the capacitance has rotation symmetry about the central axis, we have from Maxwell equation,

$$\oint \mathbf{B} \cdot d\mathbf{l} = 2\pi r B_\theta(r) = \epsilon_0 \mu_0 \int d\mathbf{S} \frac{\partial \mathbf{E}}{\partial t} = \frac{1}{c^2} \int d\mathbf{S} \frac{\partial \mathbf{E}}{\partial t}. \quad (36)$$

Therefore,

$$\mathbf{B}(r) = \begin{cases} \frac{r}{2c^2 d} \frac{dV(t)}{dt} \mathbf{e}_\theta & (r < a) \\ \frac{a^2}{2c^2 r d} \frac{dV(t)}{dt} \mathbf{e}_\theta & (r > a), \end{cases} \quad (37)$$

where $\frac{dV(t)}{dt} = (-200\pi \times 200 \sin 200\pi t) \text{ V/s}$, whose amplitude is $40000\pi \text{ V/s}$. B reaches its maximum at $r = a$. With actual numbers plugged in,

$$|B_{\max}| = \frac{a}{2c^2 d} \left| \frac{dV(t)}{dt} \right| \quad (38)$$

$$= \frac{2\text{cm}}{2 \times (3 \times 10^8 \text{ m/s})^2 \times 4\text{cm}} \times 40000\pi \text{ V/s} \quad (39)$$

$$= 1.11 \times 10^{-13} \text{ T}. \quad (40)$$